

# Summary MF2043 - Robust Mechatronics

Adam Lang

December 21, 2015

## 1 Development models

### 1.1 V-Model

The V-Model is used when developing new products. It is a way to model both hardware and software and is used broadly in the industry. It has its name from its v-shape where the horizontal axis represents time and the vertical axis represents level of abstraction.

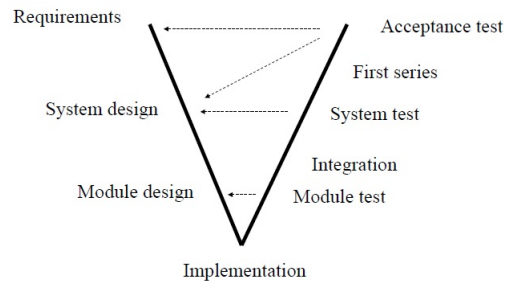


Figure 1: Graphical representation of the V-Model

There are seven different core activities, **Requirements analysis** is the first step and there are collected by analyzing the needs of the user(s). It is important to make the requirements measurable so that it will be fairly easy to see if they have been fulfilled or not. The **system design** is where the engineers analyse the business of the proposed system from the requirements. Their job is to figure out the possibilities and techniques by which the requirements can be implemented. This is more high level than the next step, **module design** this is the lower level design where the system is broken into smaller units or modules. Each one of them is explained in detail so the programmer can start coding directly. At the bottom of the V we have the

**implementation** part where all the parts are implemented and put together into one system. After the implementation step the testing starts. First is the **module testing** where the individual module is tested. These are often UTPs (Unit Test Plans) and these are executed to eliminate bugs at code level. Next is the **integration testing** where the coexistence and communication of the modules is tested. The **system testing** is done to ensure that the expectations of the customer is met. Once the system testing is complete, there will be a **first series** done. After all this the final test is the **user acceptance testing** or UAT. These tests are done in the user environment it is supposed to operate in.

## 1.2 General mechatronic development

It is important to have the whole system in mind and to look at all disciplines when developing the system. It is important to have the software developers develop testing frameworks for the hardware early in the process and the mechanical designers to have the cabling in mind when designing the mechanical system. It is also important to see the specifications as dynamic, they will change during the work process.

## 2 Operational Amplifier

The two **golden rules** for op amps:

1. The output attempts to do whatever is necessary to make the voltage difference between the input pins zero. (It "looks" at its input terminals and swing its output terminal around so that the external feedback-network brings the input differential to zero.
2. The inputs draw no current.

### 2.1 Inverting

Let's look at the inverting amp in figure 2. With the golden rules in mind we can see that:

1. The  $+$  pin is to ground (might also be to ref) so rule 1 implies that  $-$  also is.
2. This must mean that the voltage over  $R_f$  is  $V_{out}$  and that the voltage over  $R_{in}$  is  $V_{in}$ .

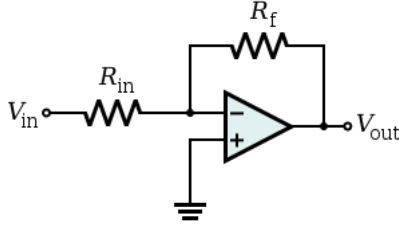


Figure 2: The inverting OP-Amp

3. Using rule 2 we have

$$V_{out} = -\frac{V_{in}R_f}{R_{in}} \quad (1)$$

So, how does this work? Let's for simplicity say that  $R_f = 100k\Omega$  and  $R_{in} = 10k\Omega$  and the input is  $+1V$ . Let's say for the sake of the matter that the output is uncooperative and sits at zero. What happens?  $R_f$  and  $R_{in}$  form a voltage divider, holding the inverting input at  $+0.91V$ . The op amp sees the enormous inbalance and forces the output to go negative. This will continue until the output is at its required  $-10V$ . At this point is both the inputs at the same voltage, ground. This also means that any tendency to lower the volt lower than  $-10V$  will pull the inverting input below ground forcing the output to rise. The downside with an inverting amplifier is the low input impedance

The - pin can be connected to a reference voltage meaning that it will use this as a virtual ground and in so "lifting" the output to an offset. This can be used when using a inverting configuration for an implementation where the sign inversion is undesired.

## 2.2 Non-Inverting

The non-inverting operational amplifier as seen in figure 3 have the desired infinite input impedance. This is almost true for most amps, some, like a JFET 411 input it would be  $10^{12}$ . The output impedance is however still a fraction of an ohm.

The simple analysis will give that  $V_- = V_{in}$  but  $V_-$  comes from a voltage divider,  $V_- = V_{out}/(R_g + R_f)$ . Set  $V_- = V_{in}$  and you will get a gain of

$$G_V = 1 + \frac{R_f}{R_g} \quad (2)$$

As seen from equation 2 the maximum gain of a non-inverting amplifier is 1. This makes the non-inverting amplifier unsuitable for some applications.

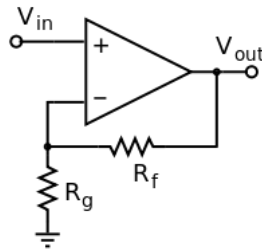


Figure 3: Non-Inverting Op-Amp

## 3 Filters

A filter is a circuit or a software that performs signal processing functions to remove frequency components from the signal, to enhance wanted ones, or both. There are many types of filters some will be covered below.

### 3.1 Analog

The analogue filter is a filter that will process the analog signal, coming straight from the hardware. The source will often be a sensor of some sort, vibration, sound, temperature, extension etc.

#### 3.1.1 Anti-alias lowpass filter

Aliasing is an effect where different signals will become indistinguishable when sampled. If a signal with noise is sampled there will be no way of differentiating the noise from the signal. There is a variety of implementations for when an analog signal will be digitized, audio being one of the most intuitive. The conversion between analog and digital is done by sampling the amplitude of the analog signal and convert each sample to a numeric quantity. This process can introduce artefacts, or misleading amplitudes due to both the finite accuracy by which the values are quantized and brought from the continuous to the discrete and from the finite rate at which these samples are taken. The **Nyquist criterion** says that the signal being digitized can not contain frequencies that exceeds half the sampling rate  $f_s$ . This is usually accomplished by passing the signal through a **anti-aliasing filter** whose cutoff frequency  $f_c$  ensures thorough attenuation of signals above the Nyquist frequency  $f_s/2$ . In short the bandwidth of the signal is restricted to satisfy the sampling theorem that states that the unambiguous reconstruction of the signal from its samples is possible if the power of the frequencies over

the Nyquist criterion is zero. In real life it is a trade off between bandwidth and aliasing.

(1) Example:

You have a signal from a sensor that you are sampling at  $f_s = 1kHz$ . What should be your cutoff frequency  $f_c$ ?

**Answer:**  $f_c = f_s/2 = 500Hz$  Due to the Nyquist criterion.

### 3.1.2 Passive filters

There are a variety of different passive filters both high- and low pass. The simplest filters are presented below.

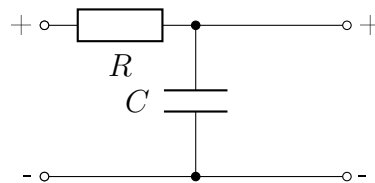


Figure 4: Passive RC low pass filter

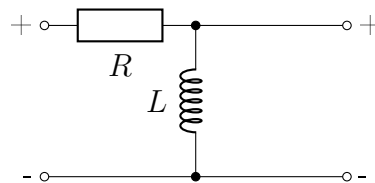


Figure 5: Passive RL high pass filter

The filters seen in figure 4 and figure 5 have counterparts for when using an RC highpass and a RL lowpass. The components will then change place and for the resistor will then connect to ground. The way the RC low pass filter works is that at low frequencies will the high reactance offered by the capacitor allow almost all of the input signal to develop as an output over the capacitors inductance,  $X_C$ . When the frequency increases will  $R$  become significantly larger than  $X_C$ . This will make the circuit attenuate the the higher frequencies and send them straight to ground. The band of frequencies that the filter will attenuate depends on the value for the components. The components relative value of  $X_C$  and  $R$  will determine how the gain,  $V_{out}/V_{in}$  is different. The gain for a passive filter is always  $< 1$

due to the out impedance beeing too high. The output voltage can be found by using

$$V_{out} = \frac{1}{(1 + \omega^2 R^2 C^2)^{1/2}} V_{in}. \quad (3)$$

The cutoff frequency for a passive filter is found as

$$f_c = \frac{1}{2\pi RC}. \quad (4)$$

The signal driving the filter sees a load of  $R$  plus the load resistance at low frequencies, dropping to just  $R$  at high frequencies. The worst case source and load impedance of an RC filter are both equal to  $R$ .

### 3.1.3 Active Filters

Active filters ar mainly to gain the amplitude of the the signal. Since a pas-sive filter will result in a voltage drop the active filter might be used where the signal needs to be amplified. This can be useful if the signal source e.g. a sensor, feeds very little signal. It us also useful due to the fact that is can feed more current than the source can. The active filter is most often built of an operational amplifier.

A **first order active low pass filter** will be a inverting amplifier and a capacitor in parallel with  $R_2$  as seen in figure 6 This will have the amplifica-

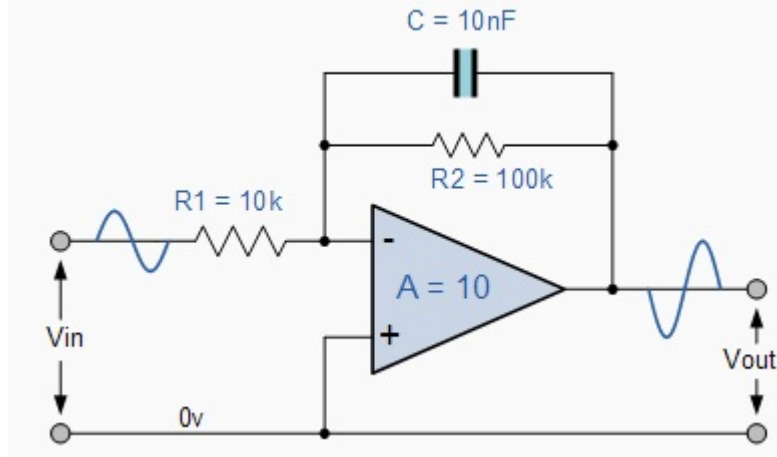


Figure 6: Inverting first order active low pass filter

tion,

$$A_{Ninv} = -\frac{R_2}{j\omega CR_1 R_2 + R_1} \quad (5)$$

and the cutoff frequency,

$$f_c = \frac{1}{2\pi R_2 C}. \quad (6)$$

The non-inverting amplifier have the advantage of having a very high impedance

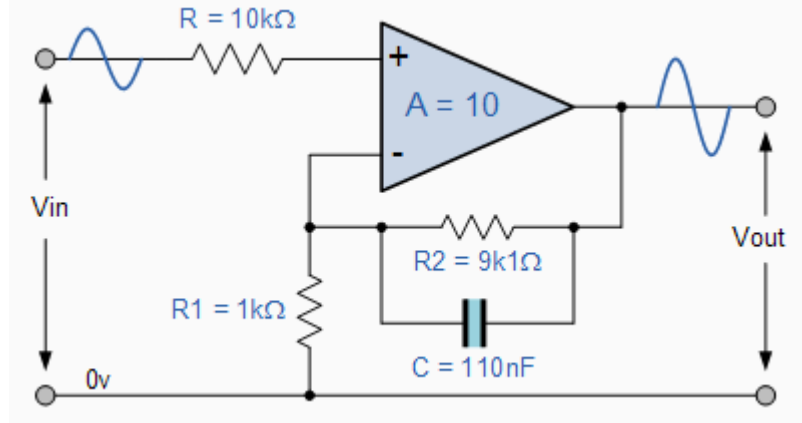


Figure 7: Non-Inverting first order low pass filter

between the input pins. But the same problem as previously discussed applies here, the lowest amplification is 1, meaning that the amplifier can not be used to damp a signal. This solution will also filter quite badly with low amplifications.

A thing to keep in mind when designing active filters is that resistors and capacitors must be provided after the set filter characteristics.

### 3.1.4 Higher order active low pass filter

The Sallen-Key low pass filter is the basis for many of the well known filters such as **Butterworth**, **Bessel** and **Chebyshev** filters.

**Butterworth** this will give a flat frequency response in the pass band. To design a Butterworth filter, all sections have the same values of  $R$  and  $C$  given simply  $RC = 1/2\pi f_c$

**Bessel** filters have linear phase or constant group delay in the pass band. They are not that more complicated than the Butterworth. Within each section we have  $R_1 = R_2 = R$  and  $C_1 = C_2 = C$  but the  $RC$  products for each section is different and must be scaled. According to this we therefore have  $RC = 1/2\pi c_n f_c$

**Chebyshev** have a steep roll off and a ripple in the passband or the stopband. They have the same calculations as a Bessel filter.

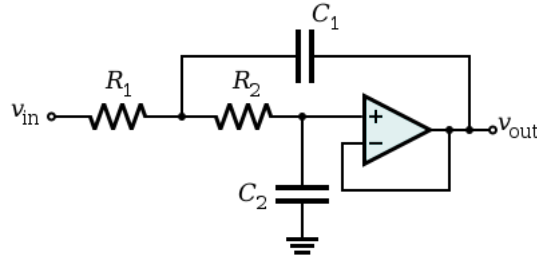


Figure 8: Second order Sallen-Key low pass filter

The filters above are in their standard configuration a second order filter. To obtain a higher order filter you simply multiply the Sallen-Key filters, this will give you an even order filter. To obtain an odd order filter you simply add one extra single order filter.

## 4 Power Supply

Due to the vast number of different power sources, ranging from the socket in the wall to solar panels and fuel cells. There is an obvious need for converters and regulators. The regulators can convert AC to DC, DC to DC (regulating) or invert from DC to AC.

### 4.1 Linear Regulator

The linear regulator is generally a linear control element in series with the DC input. This is then regulated with a feedback to have a constant output. The linear regulator is still widely used for its low noise output in applications where there is a need for precise output. The disadvantages with the linear regulator is its low effectiveness due to power dissipation in the control element. This will introduce the need for heatsink and result in wasted power. The output is always lower than the input.

### 4.2 Switching Regulator

In the switched regulator, a transistor is operated by a saturated switch (oscillator) that periodically applies the full unregulated voltage across an inductor for short intervals. The inductor's current builds up during each pulse storing  $E_L = 1/2LI^2$  in its magnetic field. When the switch is turned off, some or all of the stored energy is transferred to a filter capacitor at the output which



also smooths the output. Like the linear regulator, a feedback compares the output with a voltage reference, but it's the oscillator that controls the output by changing the oscillator frequency. The switcher is nowadays widely used in all types of electronic applications. Since the control element is either off or saturated, there is very little power dissipation. This efficiency is good since less losses means that the components can be made smaller due to the fact that less heat is generated. The downside is that the output is considerably more noisy than the linear regulator due to the switching.

#### 4.2.1 Step down (buck) converter

The switch is usually a MOSFET and the diode is used as a rectifier.  $V_{out} < V_{in}$  When the switch is closed,  $V_{in} - V_{out}$  is applied across the inductor caus-

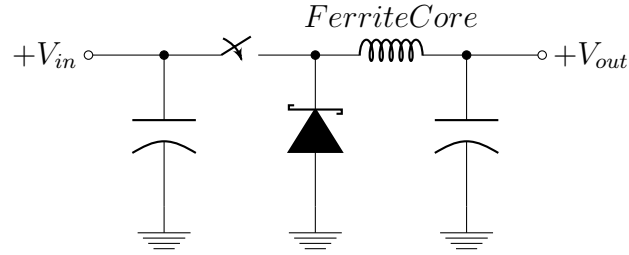


Figure 9: Buck (step-down) converter

ing a linear increasing current  $dI/dt = V/L$  to flow through the inductor. When the switch opens, inductor current continues to flow in the same direction with the "catch diode" now conducting to complete the circuit. The inductor now has a fixed voltage  $V_{in} - V_{diode}$  across it, causing the current to decrease linearly. The output capacitor acts as a smoother of the inevitable sawtooth ripple. The larger the output capacitor is, the smaller the ripple voltage. To complete the circuit in figure 9, a feedback loop should be added controlling either the pulse, or the repetition rate that compares the output to a reference. The duty cycle can be found as,

$$D = \frac{V_{out}}{V_{in}} \quad (7)$$

It will have lower  $V_{pp}$  ripple than the boost mode and can have a higher power output, up to kW.

#### 4.2.2 Step up (boost) converter

The switch is usually a MOSFET and the diode is used as a rectifier.  $V_{out} > V_{in}$

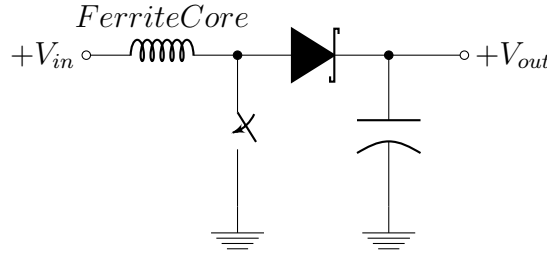


Figure 10: Boost (step-up) converter

The switching regulator can, unlike the linear, produce output voltages higher than the input voltage. When the switch is conducting, the inductor ramps up. When the switch is turned off, the inductor tries to maintain constant current, and the voltage rises rapidly. The diode turns on and dumps current into the capacitor. The output voltage can therefore be much larger than the input voltage. The duty cycle for the boost converter can be found as,

$$D = 1 - \frac{V_{in}}{V_{out}} \quad (8)$$

The boost mode converter can be used when  $P_{out} < 150W$ . The boost mode can be driven in continuous and discontinuous mode, with a bigger ripple for the discontinuous one and this is also the most common. Continuous can get unstable.

#### 4.2.3 Isolated DC-DC converters

Transformers and optocouplers provide galvanic isolation but this might also be done with a physical barrier on the PCB. This will minimize creeping and will work up until the voltage can creep through the air with a spark or find a conductive way on the PDB.

#### 4.2.4 Buck-Boost

The Buck Boost converter will allow overlap of input and output voltage range. This might be particularly useful in a battery powered unit. Say you have two AA batteries starting their life at 3V and ending it at 1.8V, here is an obvious implementation for the buck-boost regulator.

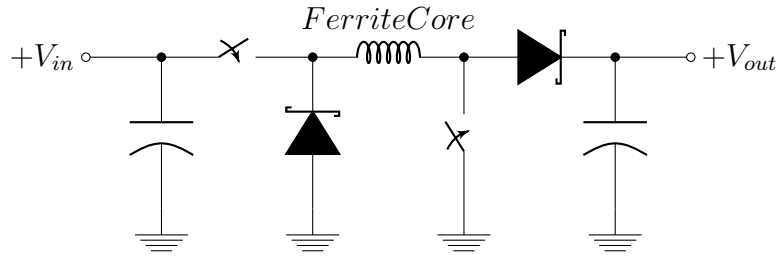


Figure 11: Non-inverting Boost-Buck converter

### 4.3 Voltage reference

There might be situations where a reference voltage is needed. There are a number of applications where a precision reference is needed, e.g. A/D or D/A conversion, waveform generators or meters etc. There are two styles of voltage references, **2-terminal** (shunt) and **3-terminal** (series). The two-terminal acts like a zener diode, maintaining a constant voltage drop when current is flowing, thus the external circuit must maintain a stable operating current. The three-terminal reference ( $V_{in}$ ,  $V_{out}$  and  $GND$ ) act like a linear regulator with internal circuitry taking care of biasing the internal reference (zener or something else).

#### 4.3.1 Zener diode

The zener diode is working much like a regular diode operated in the reverse-bias region. And will generally allow significant current if it is reverse biased above its breakdown voltage. The reverse bias is when the p-n junction is operated in reverse, meaning the voltage will basically draw the holes in the p-junction (in the p-n junction) further away from the junction and in so increasing the width of the depletion zone and increasing the voltage barrier. There is some downsides to the zener diode, it is very sensitive to temperature fluctuation and the voltage tolerance is poor except with expensive high precision zeners.

### 4.4 Thermal characteristics

The regulator is very much in need for temperature awareness.  $P_{in} - P_{out}$  gives the power consumed by the regulator but this does not make it obvious for how to calculate the temperature inside the circuit. The temperature also controls the maximum current out, the more power the regulator consumes, the less current will come out from the regulator.

Heatsinks is widely used to get rid of the increased temperatures in the circuits and components. The heatsink might be complemented by a fan or some smart construction making the box work with the chimney effect. The temperature of a die can be calculated with,

$$T_{j(max)} = P_D(R_{\Theta JC} + R_{\Theta CS} + R_{\Theta SA}) + T_A, \quad (9)$$

where  $j$  is the die,  $JC$  is the junction to case,  $CS$  is the case to heatsink,  $SA$  is the heatsink to ambient and  $T_A$  is the ambient temperature.

## 4.5 Supply protection

The powersupply needs to be protected against high voltages, reversed voltage, transients etc. Some regulators have built in protection, and others need the protection externally. The protection against reversed polarity is not always there, there is a famous example of the High-Tech Aurora 9 RC airplane radio controller who got burnt time after time again. One of the simplest way of having a reversed polarity protection is to have a diode or a couple of diodes like in figure 12 Even though the diode is a great tool, one should

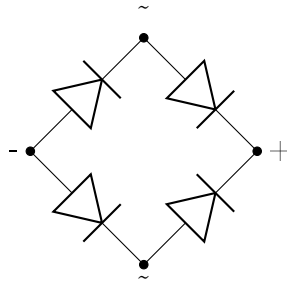


Figure 12: Reverse polarity protection with diodes

not forget that the diode will have a 0.7-1V drop over it.

## 5 Capacitors

There is a vast variety of capacitors to choose from, here is some of them with their typical application. They are typically used for protection against transients and can reduce noise.

1. Plastic foil capacitor generally have low cost and resistance but will only work in lower frequencies and will(except polypropylene) have stability

problems. They are typically used for decoupling, filters and timing circuits.

2. Ceramics are often very stable, they work well in high temperatures and over all frequencies but are more expensive. They are used in applications like oscillators and where demands for high frequency is needed.
3. Electrolytic capacitor have both wet and dry type. Wet are used for high C and V but have a high ESR (Equivalent series resistance) and the electrolyte evaporate, causing them to age. The wet type are typically used in power supplies. The dry type age well, have lower ESR and are smaller in size. Since they are used with high voltage they can cause fire, and send backwards voltage, less with higher temperatures.
4. Tantalum electrolyte ( $\mu F$  or  $pF$ )